

# Experiment 1



भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

Bachelor of Technology  
Department of Electrical Engineering

Arjun Pavanje (EE24BTECH11005)

August 11, 2025

## 0.1 Aim

To characterize the electrical behavior of diodes, BJTs, and MOSFETs by plotting their I-V characteristics through simulations (LTspice).

## 0.2 Apparatus

Laptop


### 0.2.1 Basic Procedure

,

1. Opening components menu,



2. Modifying DC-Sweep settings,

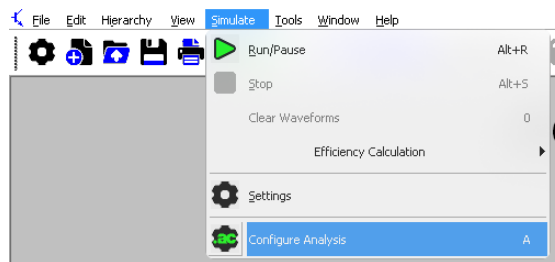


3. Running simulation,




## 0.2.2 MOSFET

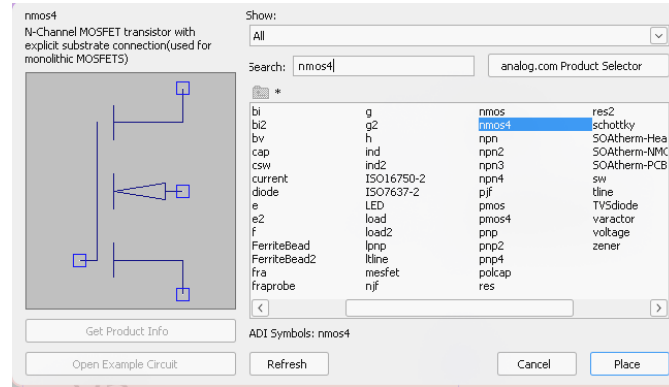
1. Select the MOSFET (shown in the figure), 2 resistors, 2 voltage sources.



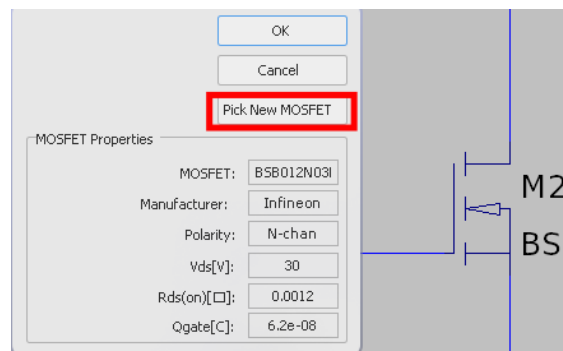
2. Select an appropriate commercially available model of the nmos,



3. Connect the circuit as shown,

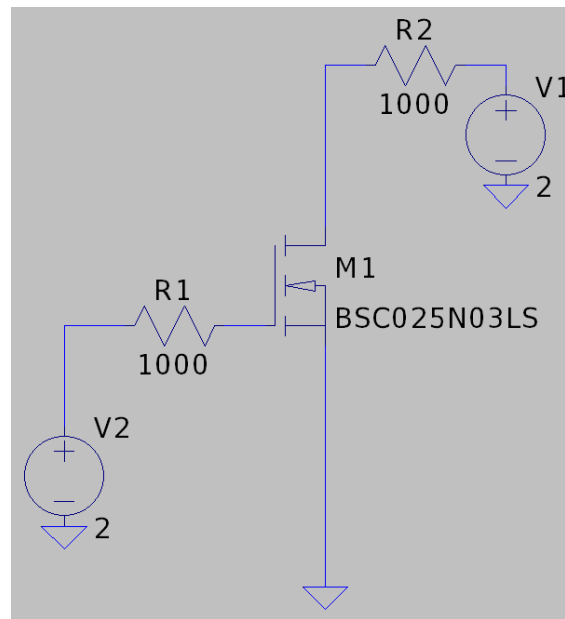

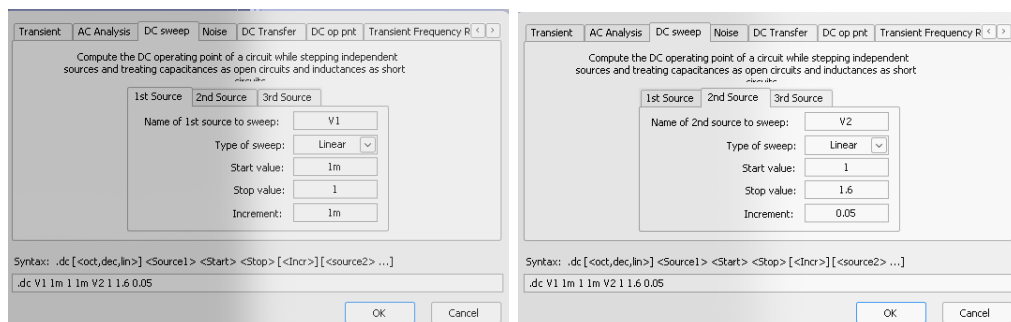
4. Configure DC sweep settings from the *Simulate* bar. These were the settings used in this case,




5. Run the simulation

### 0.2.3 BJT

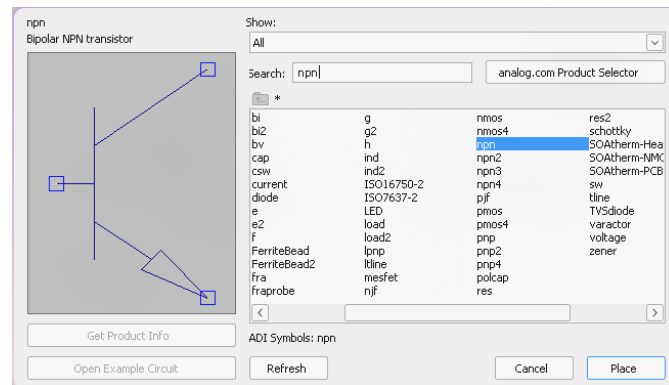
1. Select the BJT (shown in the figure), 2 resistors, 2 voltage sources.



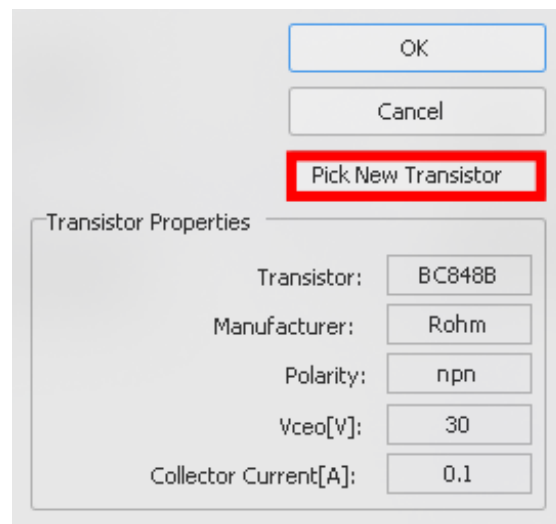
2. Select an appropriate commercially available model of the npn transistor,



3. Connect the circuit as shown,

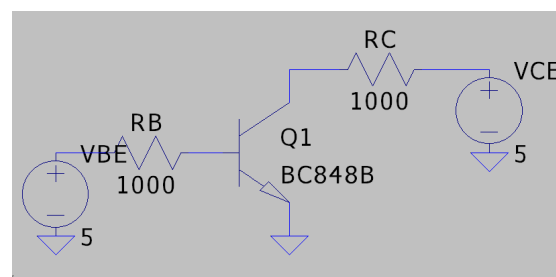

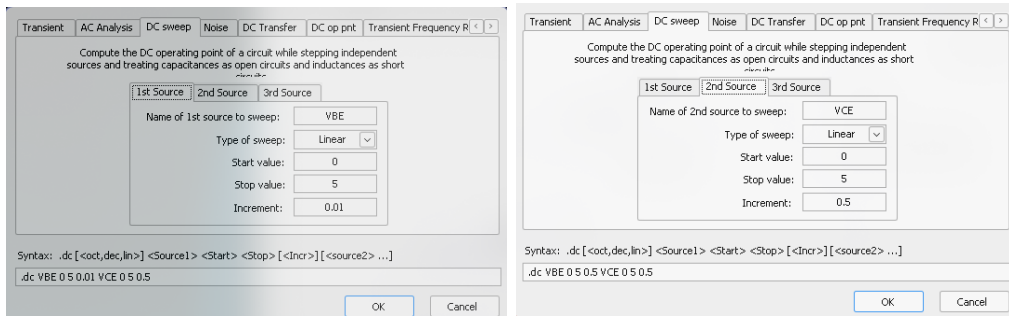
4. Configure DC sweep settings from the *Simulate* bar. These were the settings used in this case,




5. Run the simulation

## 0.2.4 Diode

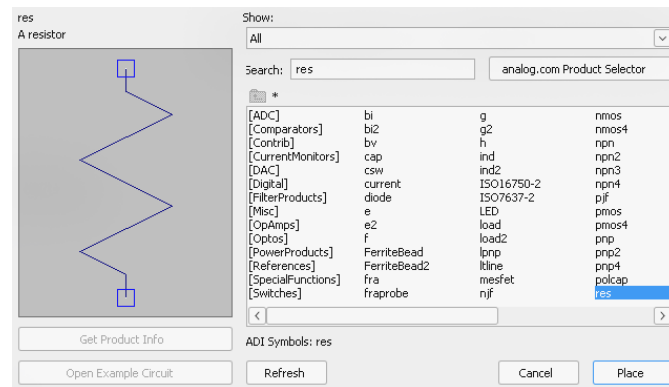
1. Select the diode (shown in the figure), a resistor, a voltage source.



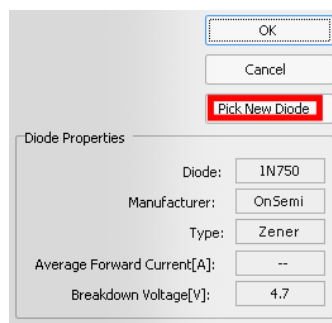
2. Select an appropriate commercially available model of the npn transistor,



3. Connect the circuit as shown,

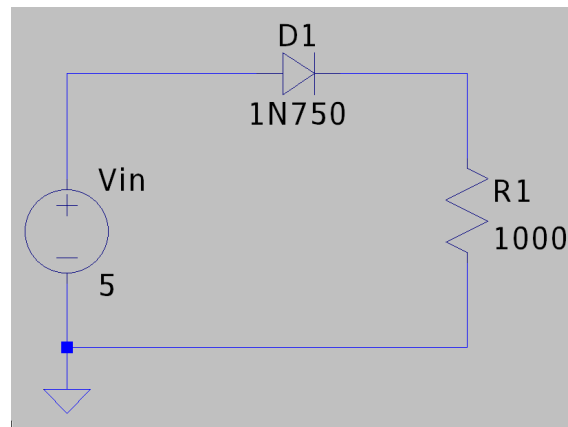

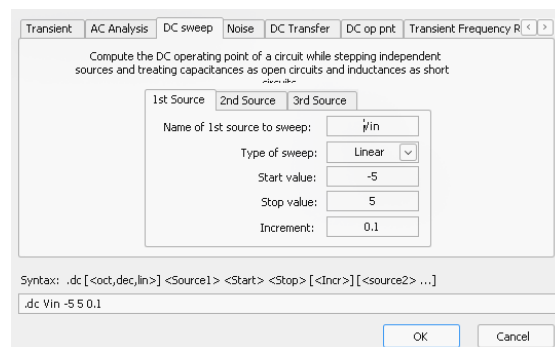
4. Configure DC sweep settings from the *Simulate* bar. These were the settings used in this case,



5. Run the simulation


## 0.3 Plots

### 0.3.1 MOSFET

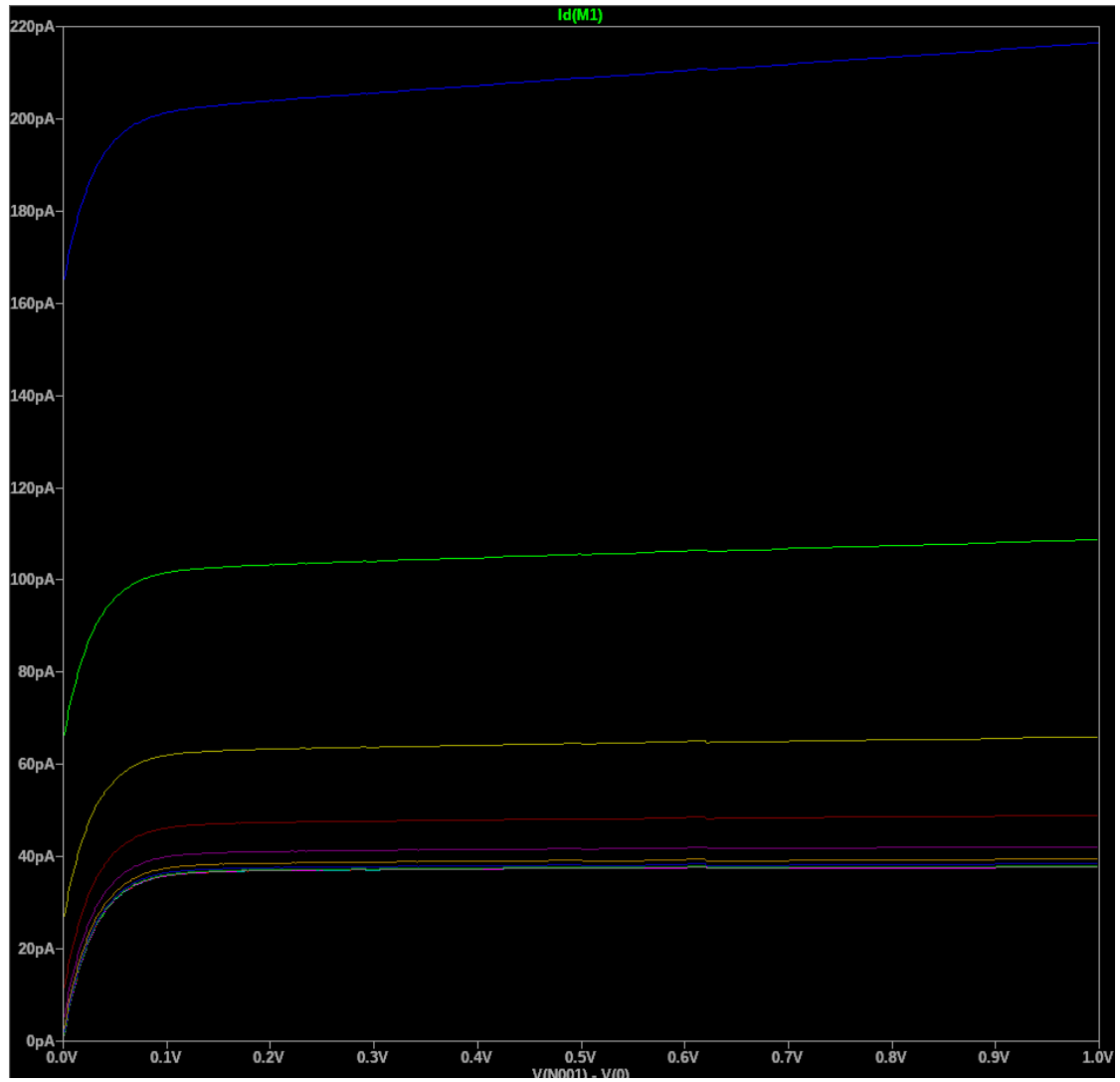




### 0.3.2 BJT

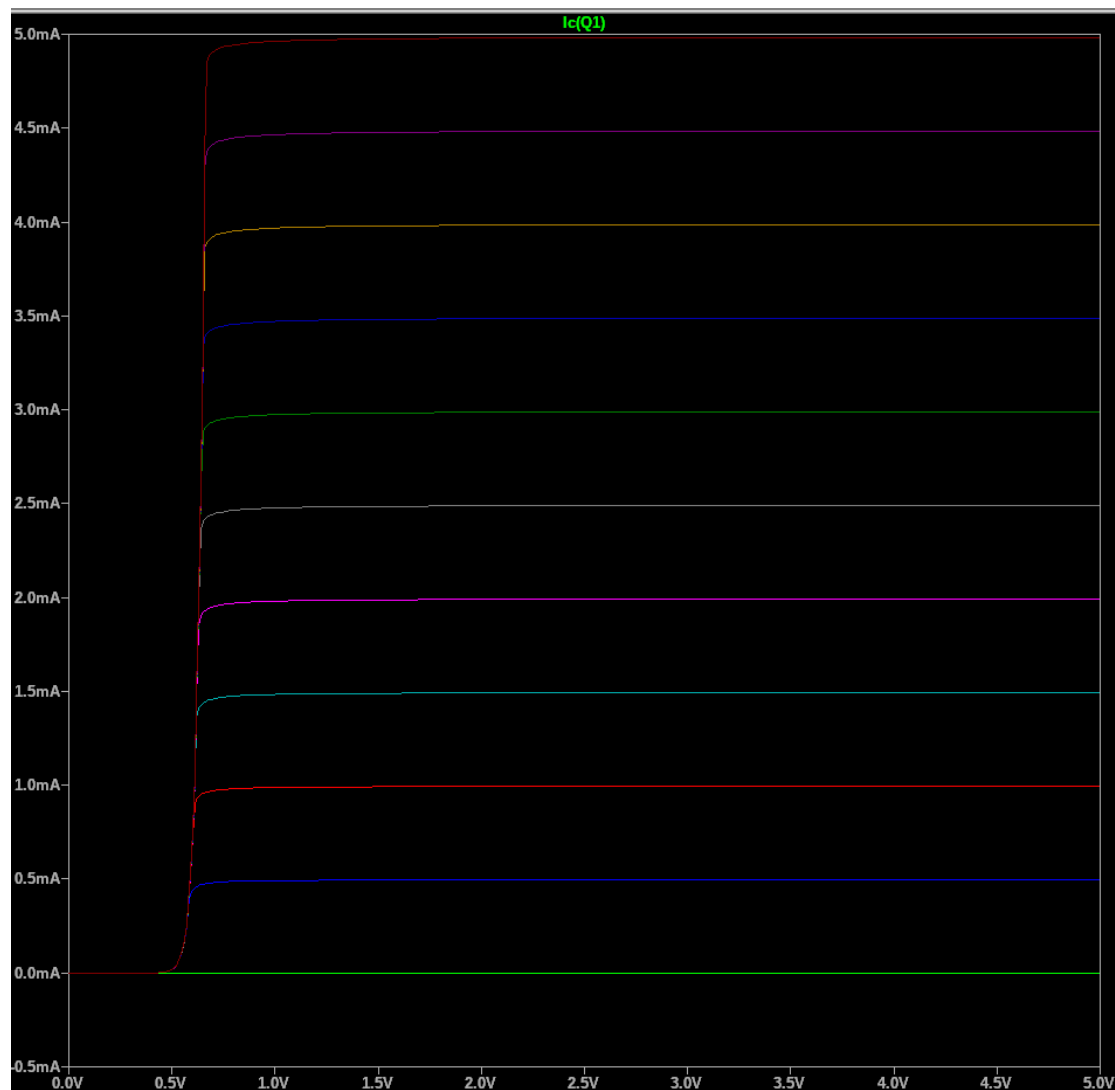

### 0.3.3 Diode

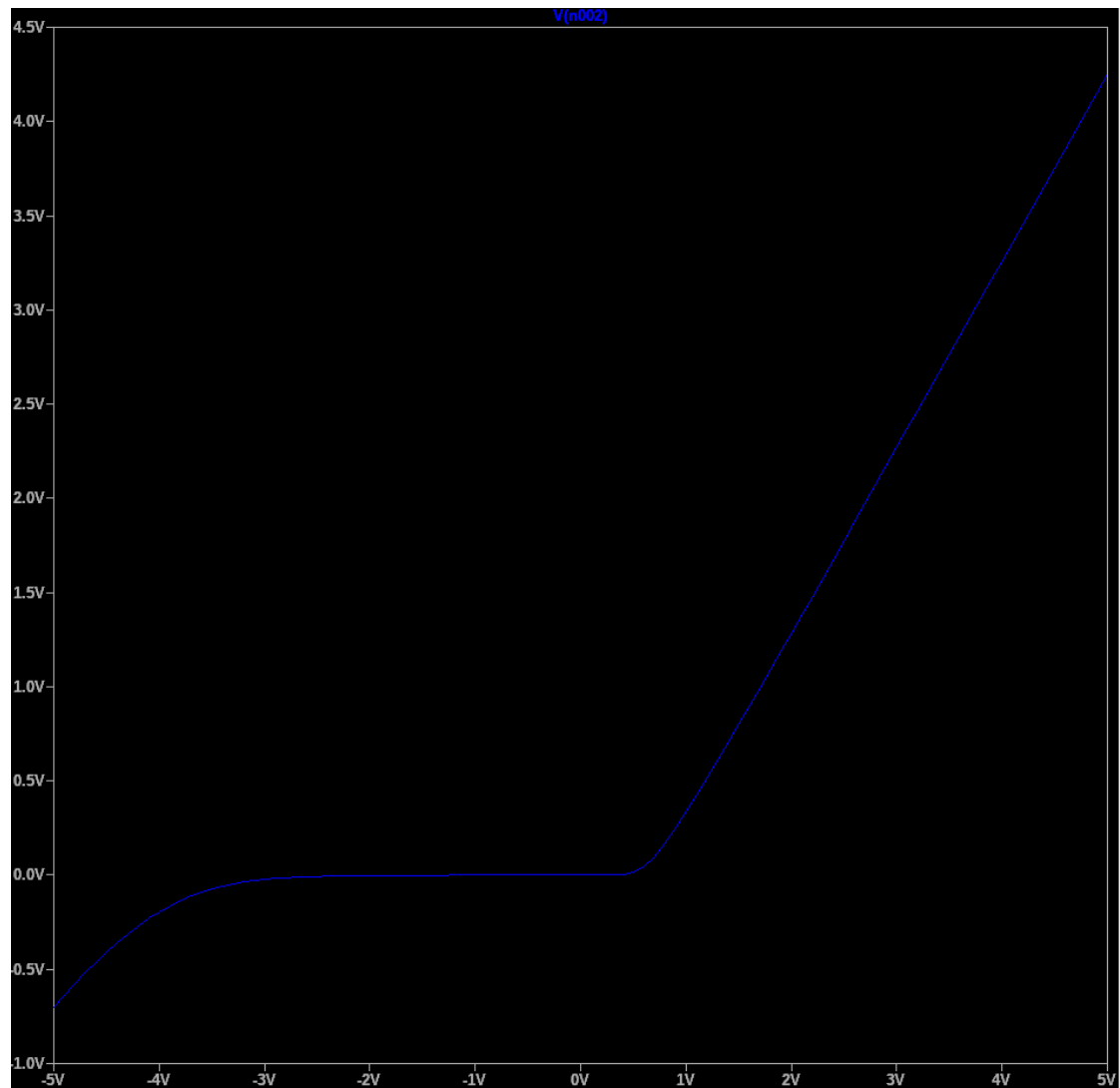

## 0.4 Conclusion

VI characteristics of MOSFET, BJT, diode have been plotted using LTspice software.