

# Lab Report: Experiment 7

EE24BTECH11003 : Akshara Sarma Chennubhatla

EE24BTECH11005 : Arjun Pavanje

October 25, 2025

## Experiment:

Plot  $I_D$  versus  $V_{DS}$  graph  
of MOSFET for different  
 $V_{GS}$  values and get  
the family of curves.



भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

Bachelor of Technology

Department of Electrical Engineering

# 1 Theory

## 1.1 MOSFET Basics

A Metal-Oxide-Semiconductor Field Effect Transistor (MOSFET) is a voltage-controlled device where the current between drain and source ( $I_D$ ) is controlled by the gate-to-source voltage ( $V_{GS}$ ). The relationship between  $I_D$ ,  $V_{GS}$ , and  $V_{DS}$  depends on the region of operation of the MOSFET.

## 1.2 Regions of Operation

**1. Cutoff Region ( $V_{GS} < V_{th}$ ):** In this region, the gate voltage is less than the threshold voltage ( $V_{th}$ ). No channel is formed and hence,

$$I_D = 0$$

The MOSFET behaves like an open switch.

**2. Triode (Linear) Region ( $V_{GS} > V_T$  and  $V_{DS} < V_{GS} - V_T$ ):** A conductive channel is formed between drain and source. The current increases linearly with  $V_{DS}$  and is given by:

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] (1 + \lambda V_{DS})$$

where:

- $\mu_n$  = electron mobility
- $C_{ox}$  = oxide capacitance per unit area
- $W/L$  = width-to-length ratio of MOSFET channel

**3. Saturation Region ( $V_{DS} \geq V_{GS} - V_T$ ):** As  $V_{DS}$  increases beyond  $(V_{GS} - V_T)$ , the channel is pinched off near the drain end. The current saturates and becomes nearly constant with  $V_{DS}$ :

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

The small increase in  $I_D$  with  $V_{DS}$  is due to channel length modulation, represented by:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

where  $\lambda$  is the channel length modulation parameter.

## 1.3 Shape of the $I_D$ – $V_{DS}$ Curves


- For  $V_{GS} < V_T$ : The MOSFET is OFF,  $I_D = 0$  (horizontal line on the x-axis).
- For  $V_{GS} > V_T$ : Initially,  $I_D$  increases almost linearly with  $V_{DS}$  (ohmic region), and then becomes almost constant (saturation region).
- Increasing  $V_{GS}$  shifts the curves upward since  $I_D$  increases with  $(V_{GS} - V_T)^2$ .

Hence, the family of curves shows:


- Steep rise at low  $V_{DS}$  (linear region)
- Almost constant  $I_D$  at high  $V_{DS}$  (saturation region)
- Separate curves for each  $V_{GS}$  value
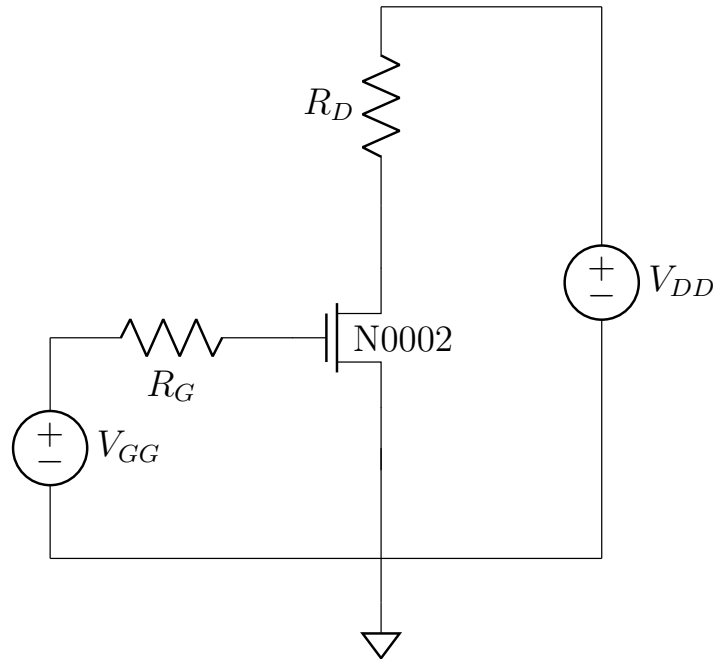
## 2 Experimental Procedure, Setup


Circuit, NMOS used was N000, and  $R_D = R_G = 150\Omega$ .



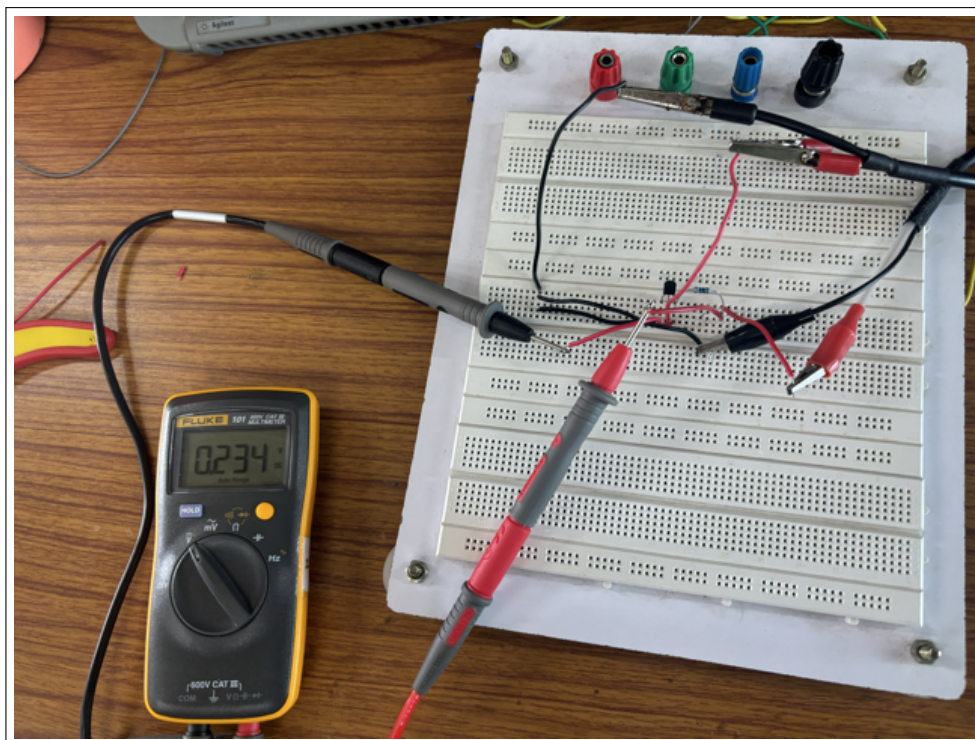1. Connect the circuit as shown
2. Figure out threshold voltage
3. Bias the MOSFET appropriately such that  $V_{GS} > V_{TO}$ .
4. Vary  $V_{DS}$  and measure  $I_D$ . Since we can't measure currents using oscilloscope, we measure potential drop across drain resistor.
5. Repeat the experiment for different values of  $V_{GS}$ .
6. Plot all the points to obtain the family of curves.




### 3 Observations and Graphs

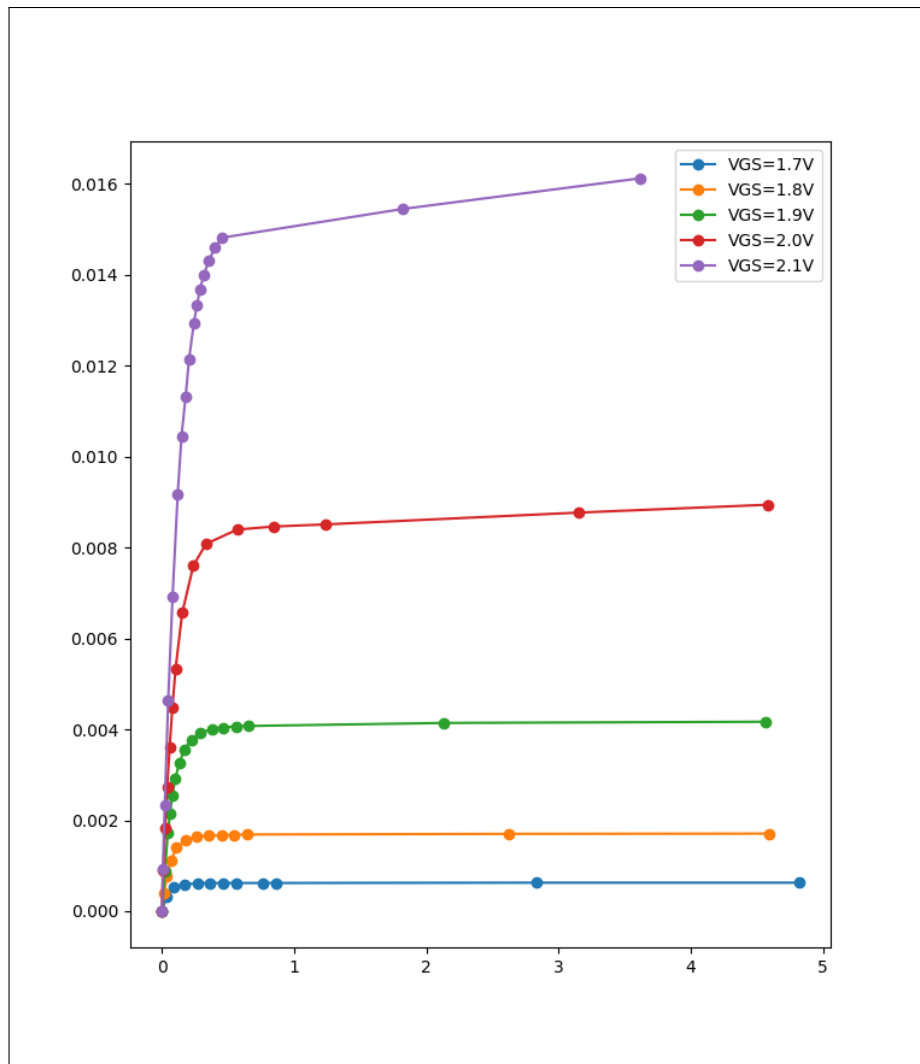

$V_{DS}$ (V)	$V_R$ (V)	$V_{GS}$ (V)	$V_{DS}$ (V)	$V_R$ (V)
$V_{GS} = 1.7 V$				
0.000	0.000		0.033	0.047
0.088	0.079		0.173	0.089
0.269	0.092		0.367	0.093
0.466	0.093		0.565	0.093
0.764	0.093		0.862	0.093
2.837	0.094		4.818	0.094
$V_{GS} = 1.8 V$				
0.000	0.000		0.017	0.060
0.039	0.116		0.069	0.168
0.112	0.209		0.179	0.234
0.262	0.245		0.355	0.249
0.450	0.251		0.549	0.252
0.645	0.253		2.621	0.255
4.598	0.256			
$V_{GS} = 1.9 V$				
0.000	0.000		0.023	0.131
0.045	0.258		0.061	0.320
0.079	0.380		0.101	0.436
0.131	0.488		0.170	0.533
0.223	0.566		0.293	0.588
0.377	0.601		0.465	0.606
0.565	0.610		0.656	0.611
2.130	0.621		4.570	0.625
$V_{GS} = 2.0 V$				
0.000	0.000		0.011	0.137
0.025	0.273		0.040	0.408
0.059	0.541		0.080	0.673
0.104	0.800		0.154	0.984
0.239	1.141		0.335	1.212
0.570	1.259		0.845	1.269
1.235	1.276		3.152	1.315
4.585	1.341			
$V_{GS} = 2.1 V$				
0.000	0.000		0.008	0.139
0.022	0.349		0.048	0.696
0.081	1.037		0.120	1.375
0.149	1.568		0.180	1.698
0.206	1.822		0.242	1.940
0.265	1.998		0.289	2.053
0.318	2.100		0.356	2.147
0.403	2.190		0.456	2.222
1.825	2.317		3.621	2.418

We can find out threshold voltage by varying  $V_{GS}$  till we get non zero  $I_D$ . For the chosen MOSFET,  $V_{TO} = 1.45V$ .

## 4 Observations

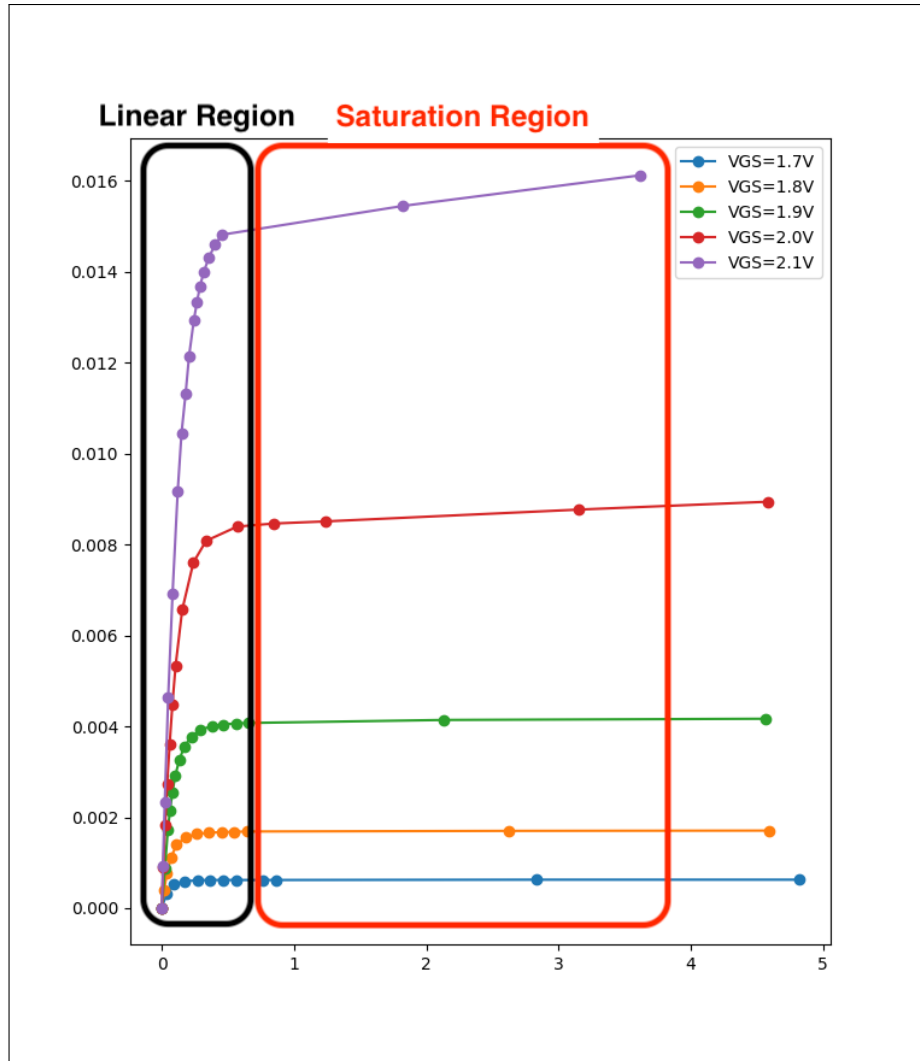

The above graph shows output characteristics of Common Source configuration of MOSFET. There are 3 regions in the graph,

- **Cutoff Region:**  $V_{GS} < V_{TO}$ , this results in the MOSFET being powered off i.e.  $I_D = 0$ .
- **Linear Region:** Also called Ohmic region,  $V_{DS}$  varies linearly with  $I_D$  (at a constant  $V_{GS}$ ) i.e. MOSFET behaves like a resistor.
- **Saturation Region:**  $V_{DS} > V_{OV}$  (where  $V_{OV}$  is Overdrive voltage).  $I_D$  is nearly constant.

## 5 Conclusion

We observe  $I_D$  vs  $V_{DS}$  characteristics of a MOSFET in common source configuration. We see all 3 operating regions of the MOSFET - Cutoff, Linear, Saturation.

Code used for plotting, [https://github.com/ArjunPavanje/EE2301/blob/main/Experiment\\_7/py.py](https://github.com/ArjunPavanje/EE2301/blob/main/Experiment_7/py.py)  
Circuit images, [https://github.com/ArjunPavanje/EE2301/tree/main/Experiment\\_7/figs](https://github.com/ArjunPavanje/EE2301/tree/main/Experiment_7/figs)